

Digital Design and Computer Architecture

Lab 5: Digital System Design – Single Path RISC Architecture – Part I


The Goal of Lab 5 is to implement R-type instructions.

We will follow the single datapath RISC architecture to achieve 2 types of operations: **ADD**, **SUB**.

1. Textbook Reading

Read Chapter 6 on R Type instructions (6.3.1)

R-type

 

and Chapter 7 on Single Cycle Microarchitecture (see the appendix for more information).

To simplify the design, we modify the original RISC instruction **op** field for I-type and R-type instructions. Here, to control the 3 MUXs and ALU (RegDst, ALUSrc, ALUControl_{2:0}, MemtoReg), we use **op**. The fields of **op** are shown below.



Examples on how to represent our operations (**ADD**, **SUB**) into R-type instructions and how the instructions work in RISC datapath architecture:

Note: Assume all the data in Register File is initialized as 0.

1. ADD in R-type instruction

ADD Register_File[1] and Register_File[2], and store the result to Register_File[6]. The first address **rs** = 1, the second address **rd** = 2, the destination address **rt** = 6;

In this case, RegDst = 1, ALUSrc = 0, ALUControl_{2:0} = 010, MemtoReg = 0, so:

op = 6'b100100

rs = 5'b00001

rd = 5'b00010

```
rt = 5'b00110
```

```
rest = 11'b0000_0000_000(shamp and funct are set as logic 0)
```

So the R-type instruction should be: 32'b100100_00001_00010_00110_0000_0000_000.

2. SUB in R-type instruction

For SUB operation, it is similar to ADD in R-type instruction. Notice that ALUControl for SUB should be 110 for ALU to do subtraction.

2.Lab Tasks

1. Implement the Register File

The module of the RISC register file should look like this:

```
module register_file(input logic clk, rst,
input logic[4:0] A1, A2, A3, //A1,A2,A3 are the address
input logic[31:0] WD3, //data from data memory
input logic WE3, //WE3 = 1, write register file
output logic[31:0] RD1, //output port one for register file
output logic[31:0] RD2, //output port two for register file
output logic[31:0] prode //prode to check the result in the register file
);

assign prode = rf_regs[1];

//.....

endmodule
```

Notice for the Register File used here, we assume there are totally 32 32-bit registers, which means the width (number of bits for each register) and depth (number of registers) are both 32.

2. Initialize the Register File

Please initialize the register file as register_file[i] = i. See Appendix 1.3. on how to initialize the register file.

3. Implement ALU

The ALU header should be:

```
module ALU(
input logic[31:0] SrcA,
input logic[31:0] SrcB,
input logic[2:0] ALUControl,
output logic[31:0] ALUResult
);

//.....

endmodule
```

Note that you only need to implement ADD and SUB operations for ALU.

ALUControl = 010, do ADD, ALUControl = 110, do SUB (see Table 5.1 in Textbook)

4. Use Testbench to verify

Please use the provided testbench to verify your design. **The instruction on how to use the testbench is posted on CANVAS/FILES.**

The testbench is targeting the provided “top.sv” module which instantiates Register File and ALU.

5. Add a “display” module

Add a display module to the provided top module to display the result from port “probe” of Register File using 7-segment display.

3. What to Turn In?

Prelab – 2 points

- Due Date: Lab 5 pre-lab report is due in the week of 10/31.

Pre-lab report:

You must submit an electronic copy of the following items (in the correct order, and each part clearly labeled) via Canvas. Submit it to the Lab 5 Pre-Lab Assignment. All items should all be included in a single file (.pdf).

1. A screenshot of your SystemVerilog Code for Register File.
2. A screenshot of your SystemVerilog Code for ALU.
3. Screenshots of your output waveforms in Modelsim
(Please set your output result radix as decimal to look clearer. It’s fine if you cannot fit in all your results in one screenshot, you can separate them into several screenshots)

Notice

For simulation, we created a waveform file for testing your Lab 5 in place of the testbench, which has been added to the Lab 5 folder in Canvas/Files. For your report, you may include EITHER the results from running the testbench OR the results from running the waveform simulation. You must use one (or both, if you’d like) of these provided methods to validate your design for the pre-lab.

In-Lab – 8 points

- Due Date: Lab 5 in-lab report is due in the week of 11/7.

In-lab report:

You must submit an electronic copy of the following items (in the correct order, and each part clearly labeled) via Canvas. Submit it to the Lab 5 In-Lab Assignment. All items should all be included in a single file (.pdf).

1. To the pdf document from your prelab assignment, **just add a section** for the in-lab assignment.
2. Take 2 pictures showing your results of ADD, SUB on the 7-segment display separately.
The ADD will be adding 2 to the **first** digit of your board number and storing result to register_file[1] (which probe signal is assigned to in the example above).
The SUB will be subtracting 3 from the **first** digit of your board number and storing result to register_file[1].
E.g. You board number is 503, for ADD, you will add register_file[2] and register_file[5] and store the result which is 7 to register_file[1] and display it through 7-segment display.

Make sure you record the board number and explain which registers you use in the in-lab report.

Appendix:

1.0. Introduction - General

For the following labs, we are going to design a simple digital system which is a demo of a modern computer with RISC architecture. Lab 5 is part 1 of the final lab, which is to implement a single datapath RISC architecture (shown below as Figure 7.9) using SystemVerilog.

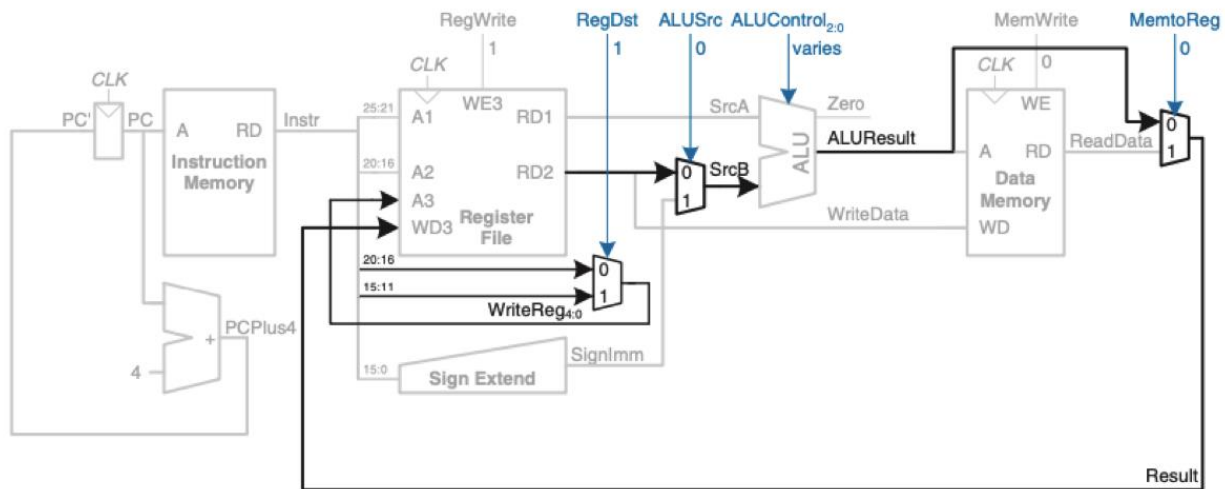


Figure 7.9 Datapath enhancements for R-type instruction

We use the **single datapath RISC architecture** to achieve 2 types of operations: **ADD**, **SUB**. These 2 operations are represented into 32-bit **R-type** machine code in modern RISC computer architecture.

R-type Instructions

ADD and **SUB** are R-type Instructions. Figure 6.5 (below) is the format of an R-type instruction. All R-type instructions have a total of 32 bits.

R-type

 


Figure 6.5 R-type machine instruction format


The fields **rs** (instr[25:21]), **rt**(instr[20:16]), **rd**(instr[15:11]) are pointers to operands. The field **op** (instr[31:26]) is used for operations. In this Lab, we will not use the **shamt** and **funct** fields, so we simply set their bits as logic 0 (instr[5:0] = 6'b000000, instr[10:6] = 5'b00000).

[Important]. The values stored in **rs**, **rt**, and **rd** are 5-bit fields that address one of 32 registers in the register file (R).

op in R-type instructions tells us to **ADD** or **SUB**. An example will be given after we explain the single datapath RISC architecture.

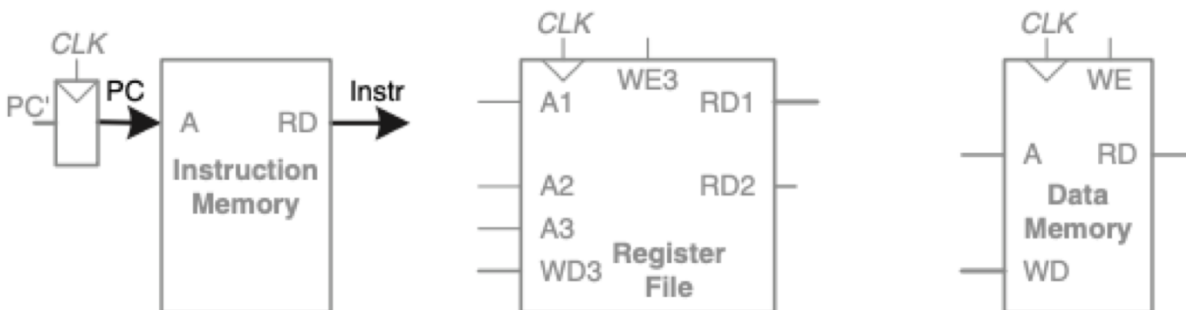1.1. Introduction - Single Datapath RISC Architecture

The main components in RISC architecture are shown below:



PC (Program Counter) contains the address of the instruction to execute.

Instruction Memory stores all the instructions. Port **A** requires the address of instructions. Port **RD** reads the instruction data. As shown here, **PC** connects to **A** and the **Instruction Memory** reads out the instruction from **RD**, labelled **Instr**.

Register File can read 2 registers and write 1 register simultaneously. For **Register File**, Port **A1**, **A2**, **A3** are the input ports for address. Port **RD1**, **RD2** are the output ports for read registers pointed to by **A1** and **A2**, respectively. **WD3** is the input port for writing data into a RF at the rising edge of the clock. **WE3** is the write enable signal port.

Data Memory stores the data. Port **A** is the address input port. Port **RD** is the data output port. Port **WD** is the data input port. Port **WE** is the write enable port.

[Important] The above figure only shows the main component of a RISC architecture. A complete single datapath RISC architecture is given in **Figure 7.9**. below.

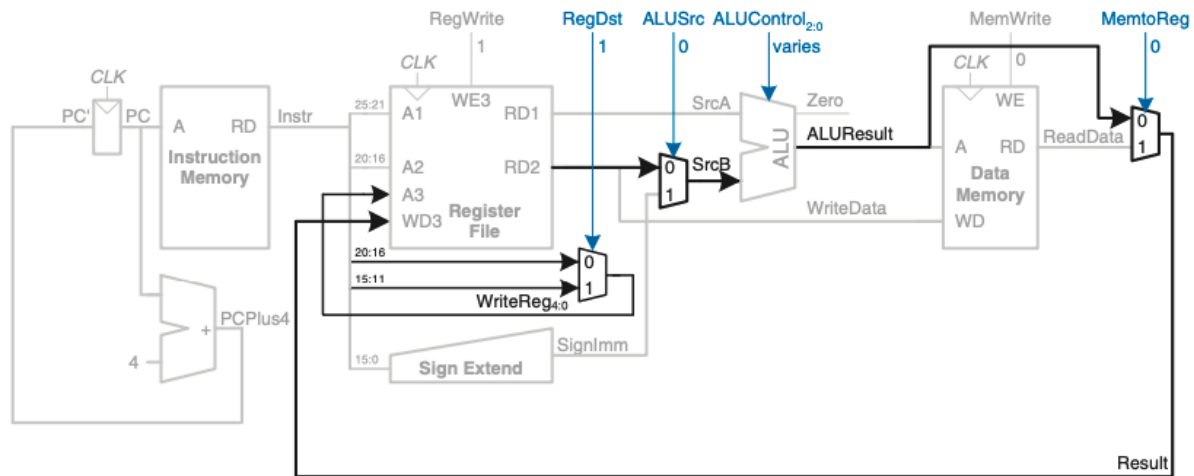


Figure 7.9 Datapath enhancements for R-type instruction

1.2. Introduction - How ADD, SUB works in RISC Architecture

Please refer to Chapter 7, Single-cycle Datapath (7.3.1) in the textbook to see how **ADD** and **SUB** work in the single path RISC architecture. Here we give you a brief description on how those operations work in the RISC architecture (for details, you still need to go over the chapters/sections in textbook stated in the beginning).

Note: To better describe it, data in Register File is represented as `Register_File[address]`. E.g. the 1st data in Register File is `Register_File[0]`

ADD and **SUB** achieved by R-type instruction, are operations for the registers in Register File. For **ADD**, `rs` (`instr[25:21]`) is input to port A1 of Register File, `rt` (`instr[20:16]`) is input to port A2 of Register File. So `Register_File[rs]` and `Register_File[rt]` are read out from port RD1 and RD2 respectively to ALU to finish the addition. The ALUResult will be inputted back to Register File (Here `MemtoReg = 0`) from port WD3. At the same time, `rd` (`instr[15:11]`) is input to port A3 of Register File. So `Register_File[rs] + Register_File[rt]` is stored in `Register_File[rd]`. For **SUB**, it is very similar, please go through the textbook section 7.3.1.

1.3. An example of initializing a register file

There are a lot of ways to initialize a register file. Here we provide the simplest way to initialize it, which is to hardcode it. Below is an example of how to initialize the register file:

```

//suppose a register file with width = 8, depth = 3
logic[7:0] registers[2:0];

always_ff@(posedge clk or negedge reset)
begin
    if(!reset) begin //active-low reset
        for(int i = 0; i < 3: i++) begin
            registers[i] <= i;
        end
    end
    else begin
        //write other logics here
    end
end

```

Please follow the example and initialize the Register File as Register_File[i] = i.